

# PHY322: Electronic Devices & Circuits

## Lab 3

Report due date: Wednesday, October 8, 2025

### AC circuits: Amplitude and Phase Relationships

In a purely resistive circuit the current and voltage will change in the same way at the same time, they are said to be “*in phase*”. However, if there are capacitors or inductors in the circuit then the current and voltage in these devices, and therefore in the circuit as a whole, will not be in phase. For a capacitor, the current leads the voltage by  $\pi/2$  as it charges/discharges, while for an inductor, the current lags the voltage by  $-\pi/2$  due to the induced back emf caused by the changing magnetic field in the inductor. For the circuit as a whole the phase difference between the current and voltage will depend on the relative sizes of the resistance  $R$  and the reactances  $X_C$  and  $X_L$ .

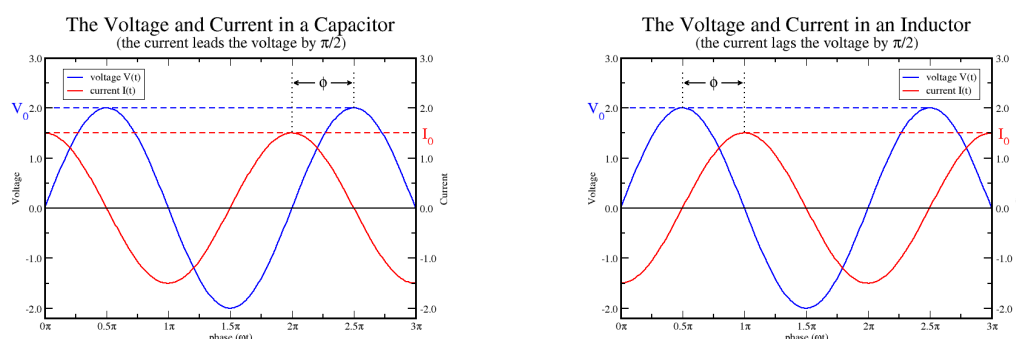



Figure 1: The voltage and current in a capacitor (left) and an inductor (right) as a function of time for a sinusoidal signal with angular frequency  $\omega$ . The phase difference between the current and voltage is labeled  $\phi$ .

#### 1. Current/Voltage Phase Difference for a Capacitor

- Design a series RC circuit that will allow you to measure, with a scope, the phase difference between the current to a capacitor and the voltage across the capacitor. Please have the lab. instructor check your circuit schematic before you build it.  
Hint #1: The scope measures voltage. What voltage will have the same phase as the current flowing to the capacitor?
- Construct this circuit with  $R = 1 \text{ k}\Omega$  and  $C = 0.02 \mu\text{F}$  and connect the appropriate signals to the scope channels.
- Using the scope, confirm that the current to the capacitor leads the voltage across the capacitor by  $\pi/2$ . Remember to save a screen image for your report.  
Hint #2: The correct triggering of the scope is essential for this measurement.

## 2. RC Time Constant

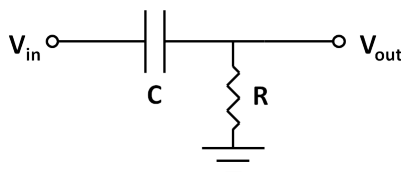- (a) Consider the following RC series circuit



Derive the relationships for the ratio  $V_{\text{out}}/V_{\text{in}}$  and the phase difference between the input and output signals, defined as

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{V_R}{V_{\text{series RC}}}$$

Note that both relationships will be a function of the signal frequency  $\omega$  and the component values  $R$  and  $C$ .

- (b) Construct the circuit with  $R = 1 \text{ k}\Omega$  and  $C = 0.02 \mu\text{F}$ . Carefully measure the component values. Set the signal generator to produce a sinusoidal waveform as  $V_{\text{in}}$  with  $V_{\text{pp}}^1 = 6 \text{ V}$ . Connect  $V_{\text{in}}$  and  $V_{\text{out}}$  to the scope.
- (c) Measure and record the signal voltages  $V_{\text{in}}$  and  $V_{\text{out}}$  and the time difference between  $V_{\text{in}}$  and  $V_{\text{out}}$  for sinusoidal waveforms with frequencies of approximately 100 Hz, 1 kHz, 10 kHz and 1 MHz. Ensure you measure the actual frequency, do not rely on the value the signal generator is set to.

| f (set) | $V_{\text{in}}$ | $V_{\text{out}}$ | $\Delta t$ | $T$ | f (actual) |
|---------|-----------------|------------------|------------|-----|------------|
| (Hz)    | (V)             | (V)              | (s)        | (s) | (Hz)       |
| 100     |                 |                  |            |     |            |
| 1 k     |                 |                  |            |     |            |
| 10 k    |                 |                  |            |     |            |
| 1 M     |                 |                  |            |     |            |

- (d) Calculate the ratio  $V_{\text{in}}/V_{\text{out}}$  from your data. Compare these values with the predicted values for this ratio at each input frequency.
- (e) The phase difference  $\phi$  between the input and output signals can be calculate using the time difference  $\Delta t$  you measured and the signal period  $T$ , with  $\phi = (2\pi)\Delta t/T$ . Calculate the phase difference for your measurements. Compare these with the predicted values for the phase difference at each input frequency.

<sup>1</sup> $V_{\text{pp}}$  refers to the peak-to-peak voltage. This is the voltage difference between the signal maximum and minimum. For a symmetric waveform, this will be  $2V_0$ .